

Chapter Six: Electricity

- **6.1 Charge and Electric Circuits**
- **6.2 Current and Voltage**
- **6.3 Resistance and Ohm's Law -
Types of Circuits**



Chapter 6.2 Learning Goals


- **Explain how current flows in an electric circuit.**
- **Define voltage and describe how it is measured.**
- **Discuss the function of a battery in an electric circuit.**

Investigation 16A

Electricity

- **Key Question:**

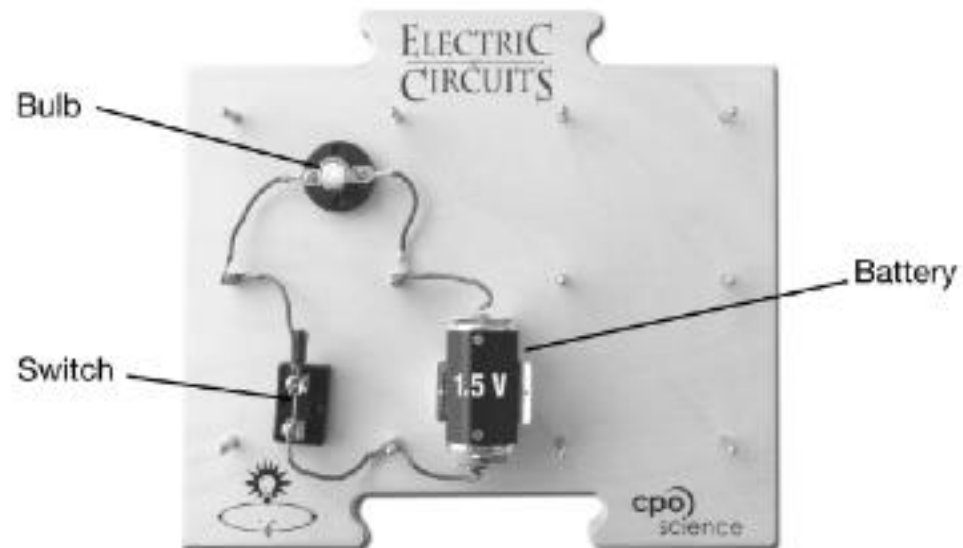How do you measure voltage and current in electric circuits?





6.2 Current and voltage

- Electric current is measured in units called amperes, or amps (A) for short.
- One amp is a flow of a certain quantity of electricity in one second.
- The amount of electric current entering a circuit always equals the amount exiting the circuit.




6.2 Voltage

- **Voltage** is a measure of electric potential energy, just like height is a measure of gravitational potential energy.
- Voltage is measured in **volts (V)**.
- A voltage difference of 1 volt means 1 amp of current does 1 joule of work in 1 second.

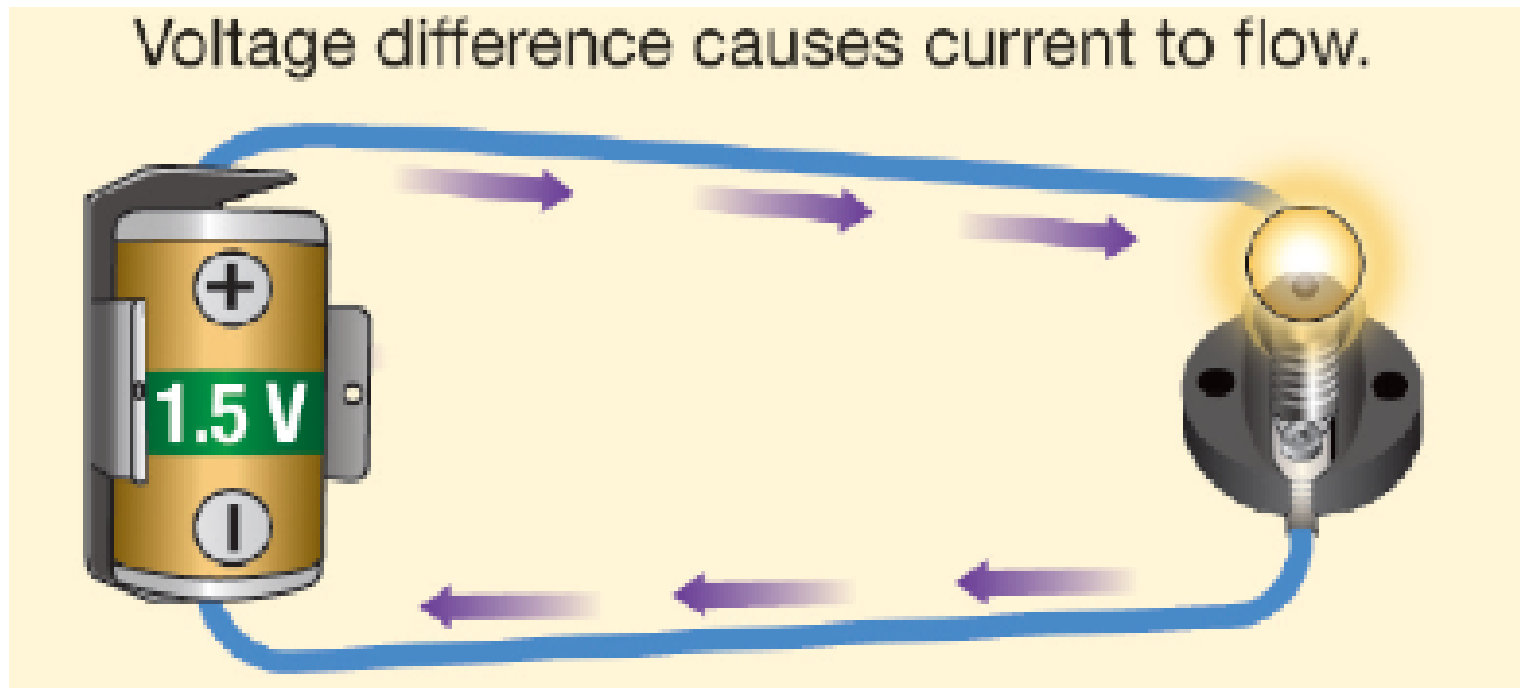
6.2 Voltage

- A difference in voltage provides the energy that causes current to flow.



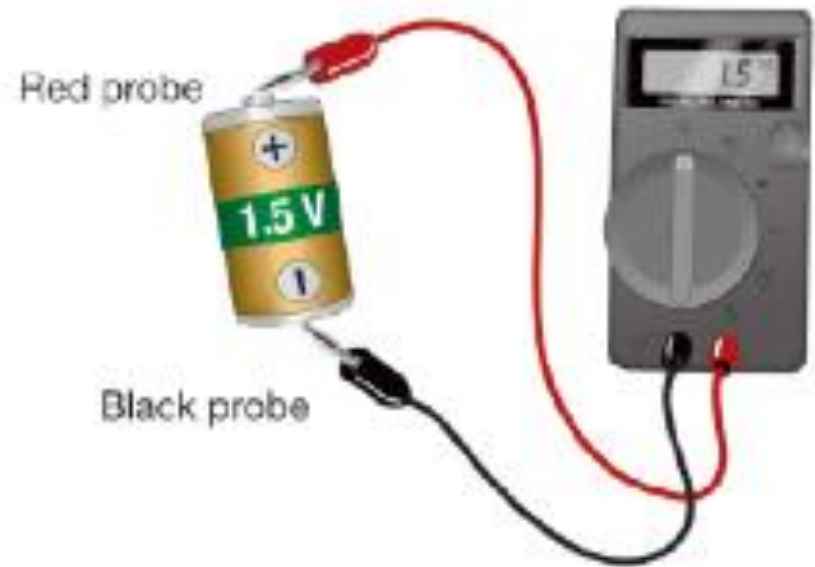6.2 Voltage

- A useful meter is a **multimeter**, which
- can measure voltage or current, and sometimes resistance.
- To measure voltage, the meter's probes are touched to two places in a circuit or across a battery.






6.2 Batteries



- A battery uses stored chemical energy to create the voltage difference.
- Three 1.5-volt batteries can be stacked to make a total voltage of 4.5 volts in a flashlight.

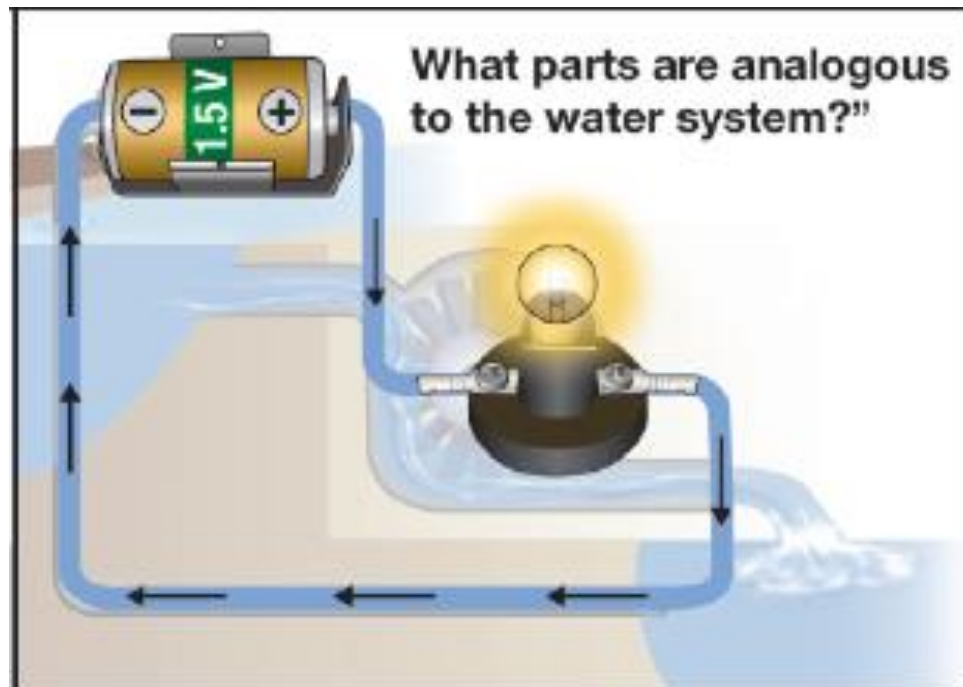
6.2 Batteries

- A pump is like a battery because it brings water from a position of low energy to high energy.





Water/Electric Circuit Analogy

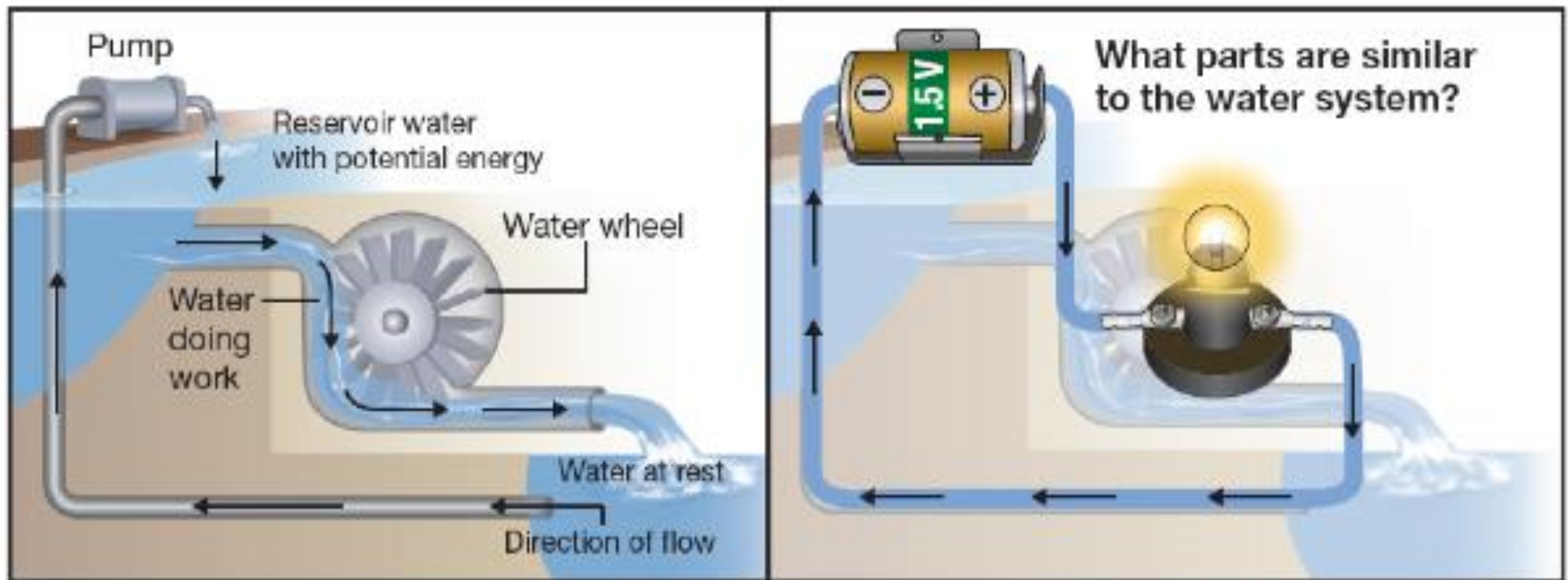



6.2 Measuring current



- If you want to measure current you must force the current to pass through the meter.
- Multimeters can measure two types of current: alternating current (AC) and direct current (DC).

6.2 Measuring current

- **Circuit breakers and fuses are two kinds of devices that protect circuits from too much current by making a break that stops the current.**

