




## Chapter 16.4 Learning Goals


- **Build and analyze series and parallel circuits.**
- **Apply Ohm's law to calculate the current in a circuit.**
- **Compare and contrast series and parallel circuits.**
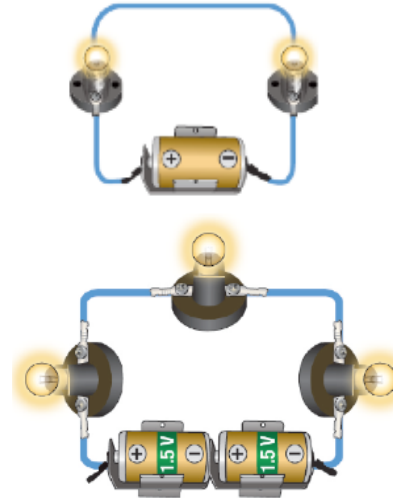
## 16.4 Types of circuits

- In a series circuit, current can only take one path, so the current is the same at all points in the circuit.



## 16.4 Series circuits

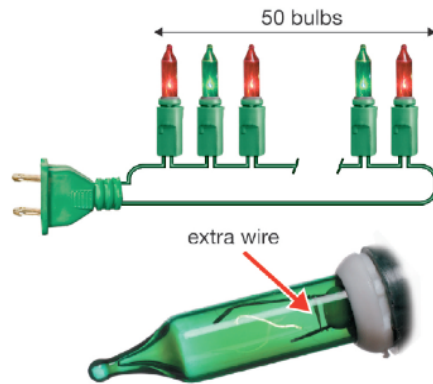


- Inexpensive strings of holiday lights are wired with the bulbs in series.
- If you remove one of the bulbs from its socket, the whole string of mini bulbs will go out.

## 16.4 Current and resistance in series circuits


- Everything has some resistance, even wires.

Adding resistances in series

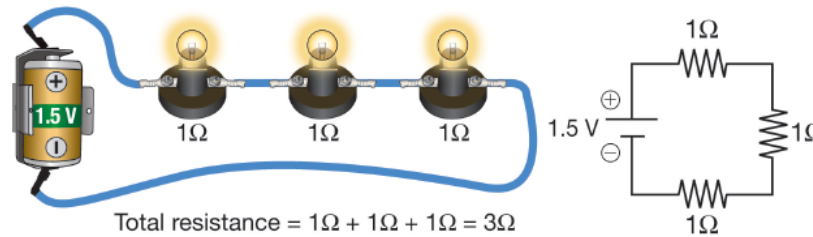

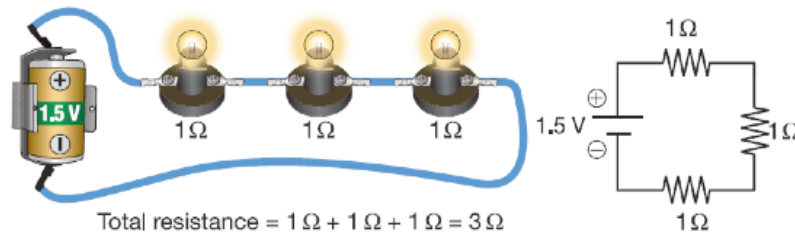
## 16.4 Current and resistance in series circuits

- If you know the resistance of each device, you can find the total resistance of the circuit by adding up the resistance of each device.



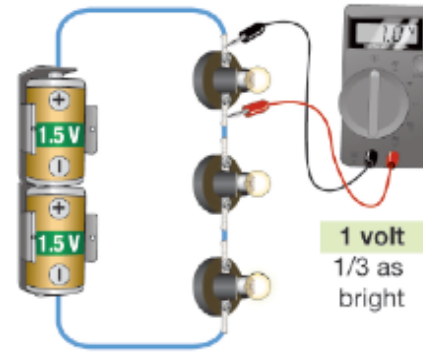
## 16.4 Voltage drop

- As each device in series uses power, the power carried by the current is reduced.
- As a result, the voltage is lower after each device that uses power.
- This is known as the voltage drop.


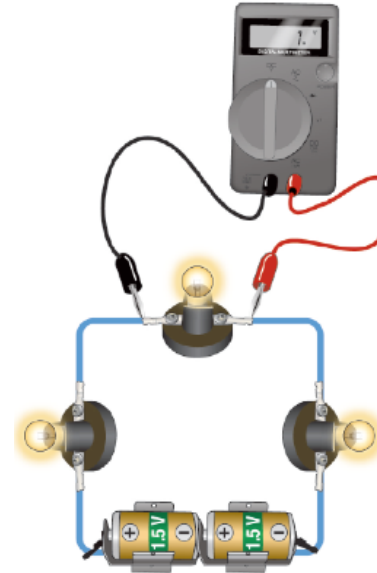
## 16.4 Voltage drop

- The law of conservation of energy also applies to a circuit.
- In this circuit, each bulb has a resistance of 1 ohm, so each has a voltage drop of 1 volt when 1 amp flows through the circuit.






## 16.4 Voltage drop and Ohm's law

- The voltage drop across a resistance is determined by Ohm's law in the form  $V = IR$ .
- The voltage drop ( $V$ ) equals the current ( $I$ ) multiplied by the resistance ( $R$ ) of the device.



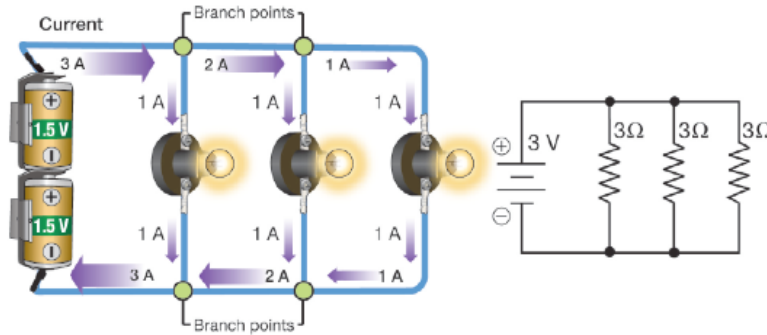
## 16.4 Parallel Circuits

- In parallel circuits the current can take more than one path.




# Parallel Circuits

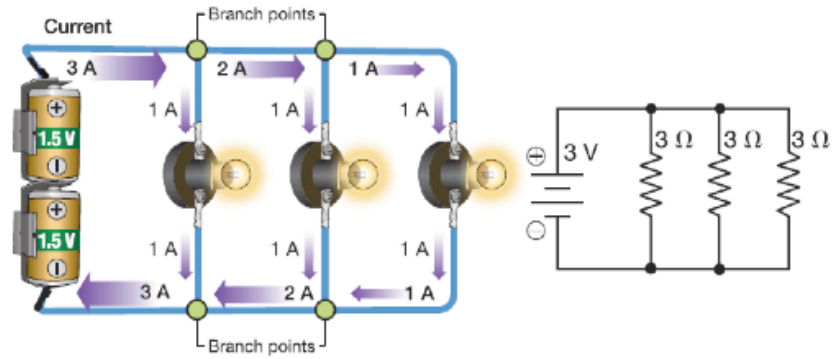

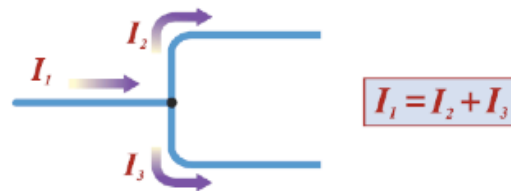
## Kirchhoff's current law

All current flowing into a branch point must flow out again.





## 16.4 Voltage and parallel circuits

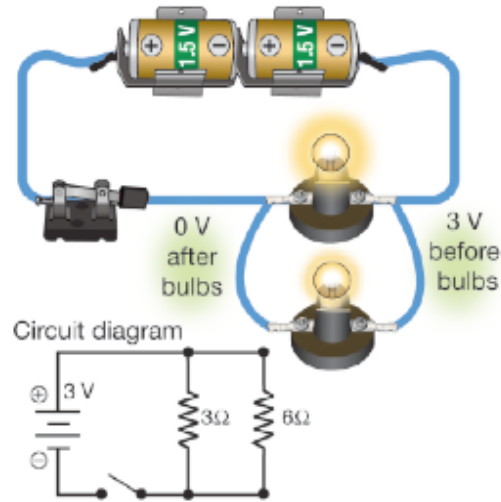

- If the voltage is the same along a wire, then the same voltage appears across each branch of a parallel circuit.



## 16.4 Voltage and parallel circuits

- **Parallel circuits have two advantages over series circuits.**
  1. Each device in the circuit has a voltage drop equal to the full battery voltage.
  2. Each device in the circuit may be turned off independently without stopping the current in the other devices in the circuit.

## 16.4 Current and parallel circuits

- Each branch works independently so the total current in a parallel circuit is the sum of the currents in each branch.

